

Pyrodetector

To desing amplification board of detector, some initial knowledge of principle of pyrodetector work is required.

A pyrodetector can be considered as a capasitor with a temperature dependent charge. The change of the surface charge ΔQ of ferroelectric material due to a small change ΔT of the temperature is given by:

$$\Delta Q = A \left(\frac{dP}{dT} \right) \Delta T = AK_p \Delta T,$$

where P is polarisation K_p -piroelectric coefficient, A - surface area of the detector element. Then, current of the detector is:

$$i_s = AK_p \frac{dT}{dt}.$$

The heat equation of the detector element when heated by the incident radiation power P is:

$$C_{th} \frac{dT}{dt} + \lambda(T - T_0) = P,$$

where T_0 is ambient temperature , P - radiative power, λ - thermal conductivity, C_{th} - thermal capacity. Let consider that an input power contain periodic component $P(1 + e^{j\omega t})$. The temperature is then described by $T = T_0 + T^* + T(\omega)e^{j\omega t}$, where $T(\omega)$ - amplitude of the oscillating temperature component and T^* is the steady state temperature increase by P. If we solve heat equation with this condition, we will get:

$$j\omega C_{th} T(\omega) + \lambda T(\omega) = P,$$

then

$$|T(\omega)| = \frac{P}{\lambda(1 + \omega^2 \tau_{th}^2)^{1/2}},$$

where $\tau_{th} = C_{th}/\lambda$ is thermal time constant. Then for current:

$$|i_s| = \frac{\omega AK_p P}{\lambda(1 + \omega^2 \tau_{th}^2)^{1/2}},$$

and for signale voltage

$$|v_s| = \frac{|i_s| R_L}{(1 + (\omega R_L C)^2)^{1/2}},$$

where C is the electrical capacitance and R_L the load or shunt resistnce which is usually much smaller than the internal resistnce of the detector (in our case more than 100 times).

Response ($|r| = |v_s|/P$):

$$|r| = \frac{\omega AK_p P}{\lambda(1 + \omega^2 \tau_{th}^2)^{1/2}} \frac{R_L}{[1 + (\omega R_L C)^2]^{1/2}}$$

It seen that for low frequencies $\omega < 1/\tau_{th}$ the response becomes

$$r = \frac{\omega AK_p R_L}{\lambda}$$

and for high frequencies, $1/\tau_{th} < \omega < 1/R_L C$, the response is constant and given by

$$r = \frac{AK_p R_L}{C_{th}}$$

The smaller the load resistance the larger the frequency range with constant response which is independent of both frequency and thermal conductivity.

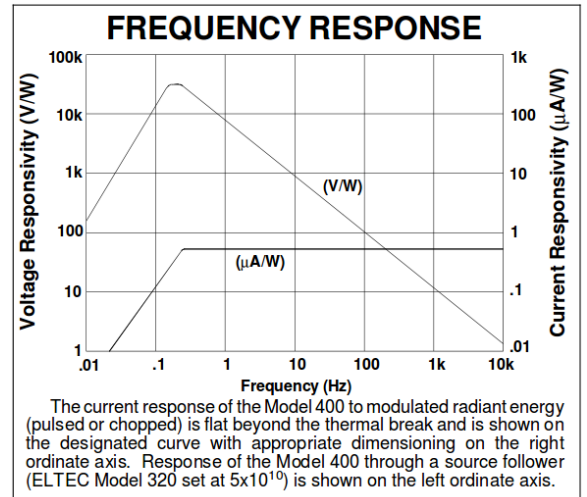


Figure 1: Response of ELTEC 400

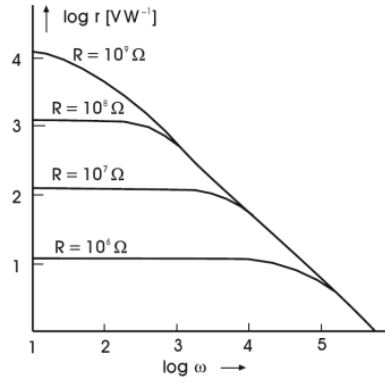


Fig. 3.5. Response for various values of load resistance. $K_p = 2 \times 10^{-4} [\text{C m}^{-2} \text{K}^{-1}]$; $C_{th} = 1.64 \times 10^{-5} [\text{JK}^{-1}]$; $C = 22 \text{ pF}$; $A = 1 \text{ mm}^2$

Figure from W.J.Wittman. *Detectors and signal processing. Technical realisation.*

On figure 1 You see response of our detector. Peak of volage response is moving (as shown above) and it depend from load resistance, but it ok in our case, because we also use 50 GOm load resistor.

Noise analysis

The noise is produced by the resistance (Jonson noise mainly from the shunt resistance) and by the thermal fluctuations. The mean square current fluctuations is

$$\langle i_n^2(\omega) \rangle = \omega^2 A^2 K_p^2 \langle \Delta T^2(\omega) \rangle .$$

For the thermal noise within the bandwidth B

$$\langle i_{nT}^2 \rangle = \frac{4k\omega^2 A^2 K_p^2 T^2 B}{\lambda(1 + \omega^2 \tau_{th}^2)}$$

The total noise current including Johnson noise becomes

$$\langle i_n^2 \rangle = \frac{4kTB}{R_L} + \frac{4k\omega^2 A^2 K_p^2 T^2 B}{\lambda(1 + \omega^2 \tau_{th}^2)}$$

Signal-to-noise ratio:

$$\frac{S}{N} = \frac{|i_s^2|}{\langle i_n^2 \rangle} = \frac{P^2}{\frac{4kT\lambda^2(1+\omega^2\tau_{th}^2)B}{\omega^2 A^2 K_p^2 R_L} + 4kT^2\lambda B}$$

Jonson noise is much larger than the thermal noise, so Noise equivalent power

$$NEP = \frac{4kT\lambda^2(1 + \omega^2 \tau_{th}^2)B}{\omega^2 A^2 K_p^2 R_L}$$

When the detector element is in thermal equilibrium with its surrounding, there will be zero mean power flow between them. However, it will experience a fluctuation spectrum with an RMS value. This gives the "background limit" to the detector NEP. (*Infrared Detectors and Emitters: Materials and Devices. Peter Capper, C.T. Elliott*)

Preamplifier

Transistor

To select the input transistor pre-amp should behave responsibly. Because the noise then it will create in next amp stages will amplified more and can be perceived by the useful signal. For that I select ultra-low noise ($0.8 \text{ nV}/\sqrt{\text{Hz}}$) fet transistor BF862.

In datasheet to detector was proposed to make source follower. In this case we have amplification in current but not amplification in voltage. I propose replace follower by voltage amplifier. For this I use schematic as on figure 3, but without capacitor Cs. Resistance Rg is load 50 GOhm resistor. Capacitor at the out of amplifier cut constant voltage. It must have big capacitance and there low resistance to ac component. Resistors Rd and Rs set working line and working point. Value of $R_d + R_s = R$ we get from equation:

$$V_d = V_{dd} - I_d R,$$

and value Rs, that set working point:

$$R_s = V_{gs} / I_d.$$

It is very important to choose right working line and working point, in other case we will have nonlinear amplification (look at figure 7 of bf862 datasheet).

On figure 4 red is working line and blue is working point. In this amplifier $R_s = 27 \text{ Ohm}$, $R_d = 220 \text{ Ohm}$, out capacitor 10 uF . Maximum of amplification is approximately 7 times, but in real life it is about 3,5 times. That may caused by that figure 3 from datasheet is not real. I will check it by simulating work of transistor in Multisim. The role of capacitor Cs is to help of amplification for ac signals, but now my experiments with it is not successful.

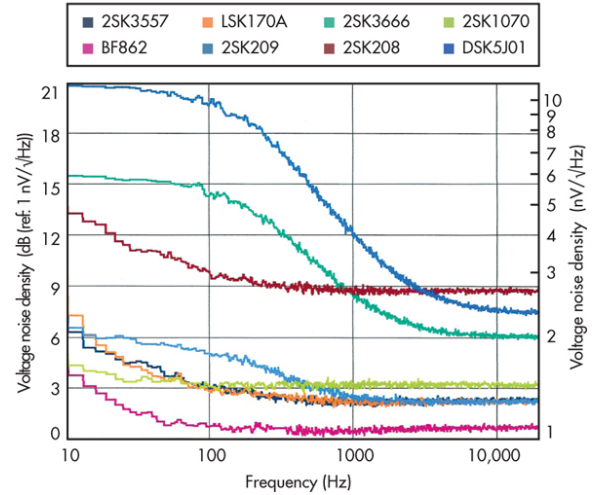


Figure 2: Noise measurements
electronicdesign.com

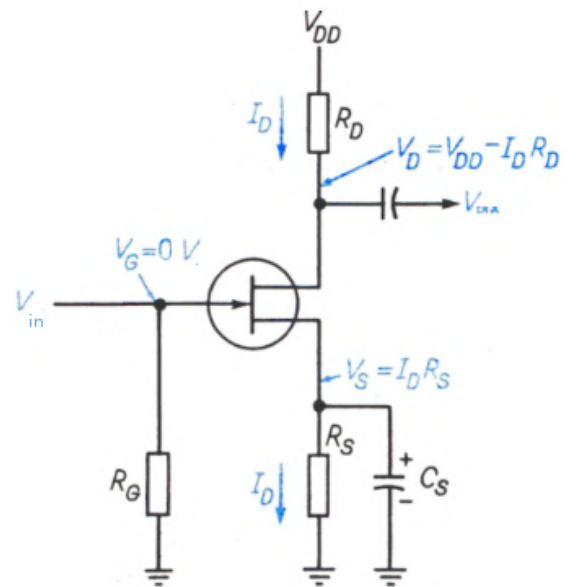


Figure 3: Typical wiring diagram
Joseph D. Greenfield. Practical Transistor and Linear Integrated Circuits


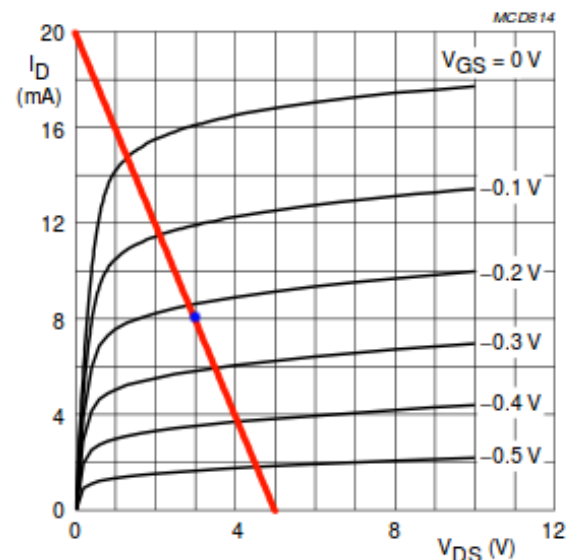


Figure 4: Drain current as a function of drain-source voltage; typical values
BF862 datasheet

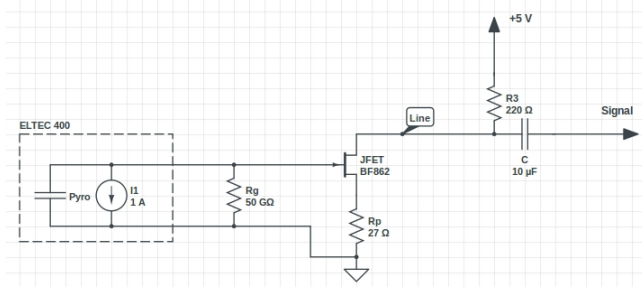

(a) Schematic of preamp



(b) Preamplifier (prototype)

Other

There are some other very important things for stable work of amplifier:

- 1) Shielding. All parts of amp must be shielded. Very sensitive is gain of the transistor, so we must check twice if this place is shielded.
- 2) Power supply. I give power supply from battery and in this case so much smaller 50 Hz component, so we must give very good and stable power for preamp.
- 3) Working with 50 GΩ is hard. So it will be fine to wash detector from flux etc and give all condition that input resistor will respond to it nominal.
- 4) If we want to work with BNC connectors, we can work only with two wires. So I propose make wire from drain of transistor slightly longer and put R_d and out capacitor on main amp board. In this case we have only 2 wires (GND and wire from drain).

Conection with board

All connection with board is realized throw RaspberryPi. For it purpose I write programs (for RP -server and UserComp - client) to communicate. Features of the work described in ReadMe files to the programs.

...to be continued...

Install requirement

To start to work with i2c and spi on raspberry first You must activate them. Open LXTerminal and enter the following command:

```
sudo nano /etc/modules
```

and add these two lines to the end of the file:

```
i2c-bcm2708  
i2c-dev
```

Then

```
sudo nano /etc/modprobe.d/raspi-blacklist.conf
```

and comment

```
blacklist spi-bcm2708  
blacklist i2c-bcm2708
```

Install this tool for testing potentiometers.

```
sudo apt-get install i2c-tools
```

To avoid having to run the I2C tools at root add the 'pi' user to the I2C group:

```
sudo adduser pi i2c
```

Reboot

```
sudo reboot
```

If You type

```
sudo i2cdetect -y 1
```

You must see 8 addresses with potentiometers.

Copy program for raspberry (that I send) and type make in this folder. Follow the instructions in ReadMe file.

Testing of the board

- 1 Check Your Power supply. It must be 12V 1-2A, GND out, positive inside. If cooler work it mean that power of board is present. If leds on raspberry blink, than power of raspberry is also present.
- 2 Connect to the raspberry. Connect raspberry to the router and You computer to this router. Find IP of raspberry (on web-page of router or with ip scanner). If there is no RP in net, check connection of raspberry (Three leds near usb on RP must be on (2 green 1 yellow)). Type on Your computer:

```
ssh -X pi@IP
```

where IP - is ip of raspberry.


- 3 Check if potentiometers is ok.

```
sudo i2cdetect -y 1
```


There must be 8 numbers strarting from 0x28. If there ansver all addresses ask me what to do (Hodnevuch@gmail.com). If there is no addresses check bus.

- 4 Start Program for raspberry and then start on You computer program for user. Follow the instructions in ReadMe files.

Enjoy! =)

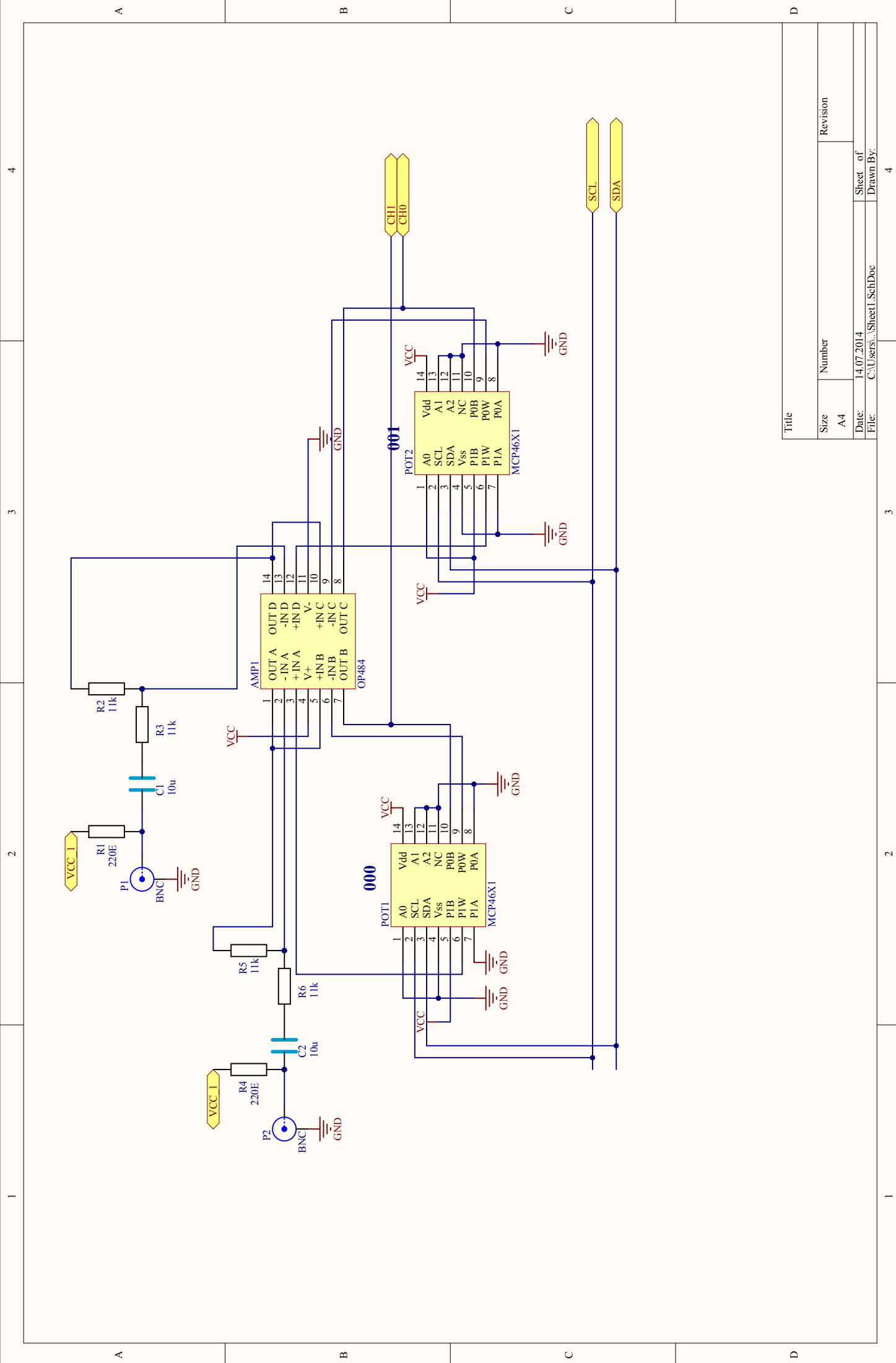


Title	
Size	Number
A4	
Date:	Revision
14.07.2014	
File:	Sheet of
C:\Users\... Sheet1_SchDoc	Drawn By:
	4

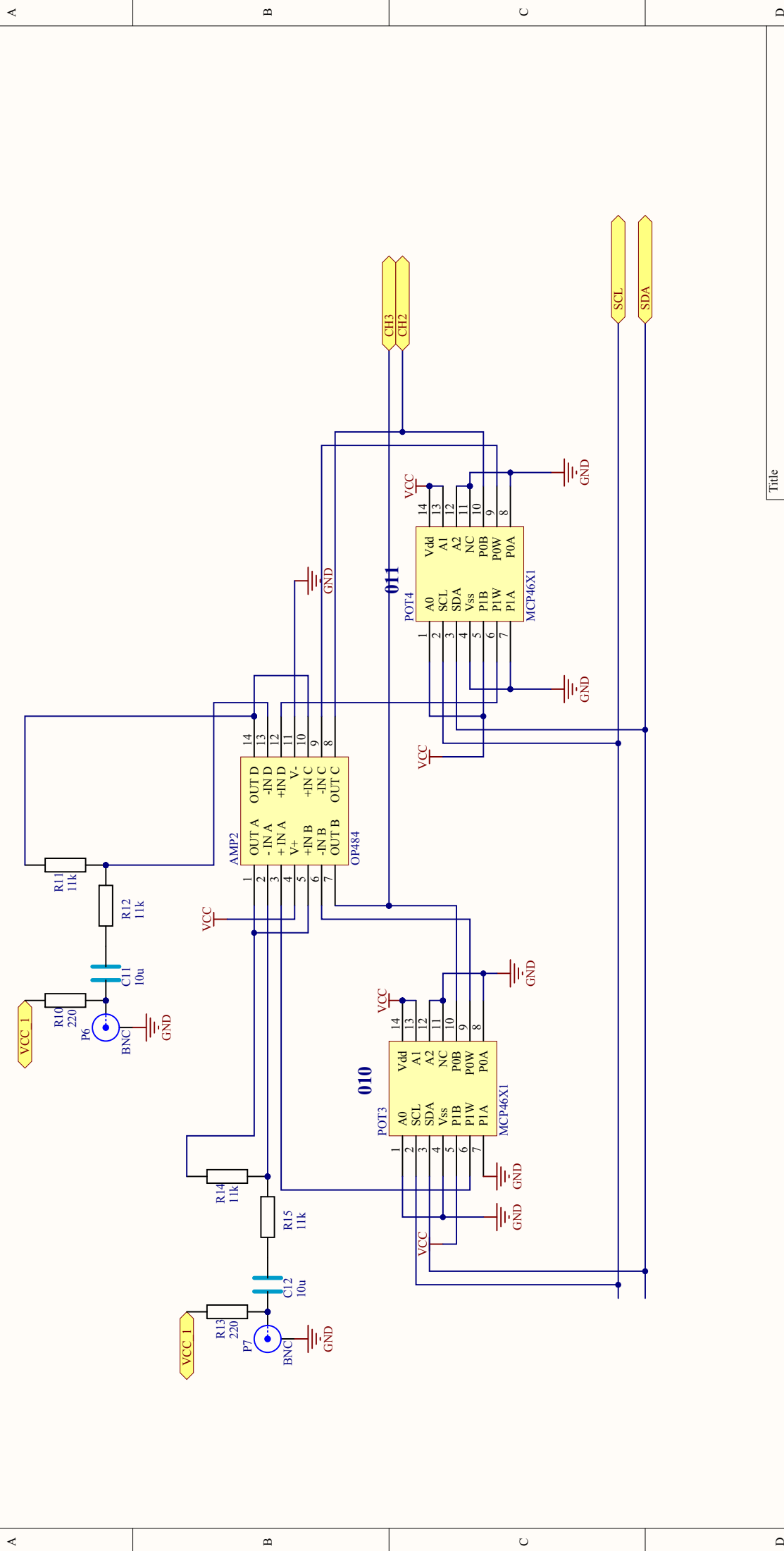

Title	
Size	Number
A4	
Date:	14.07.2014
File:	C:\Users\... Sheet3_SchDoc
Sheet of	4
Drawn By:	

Revision

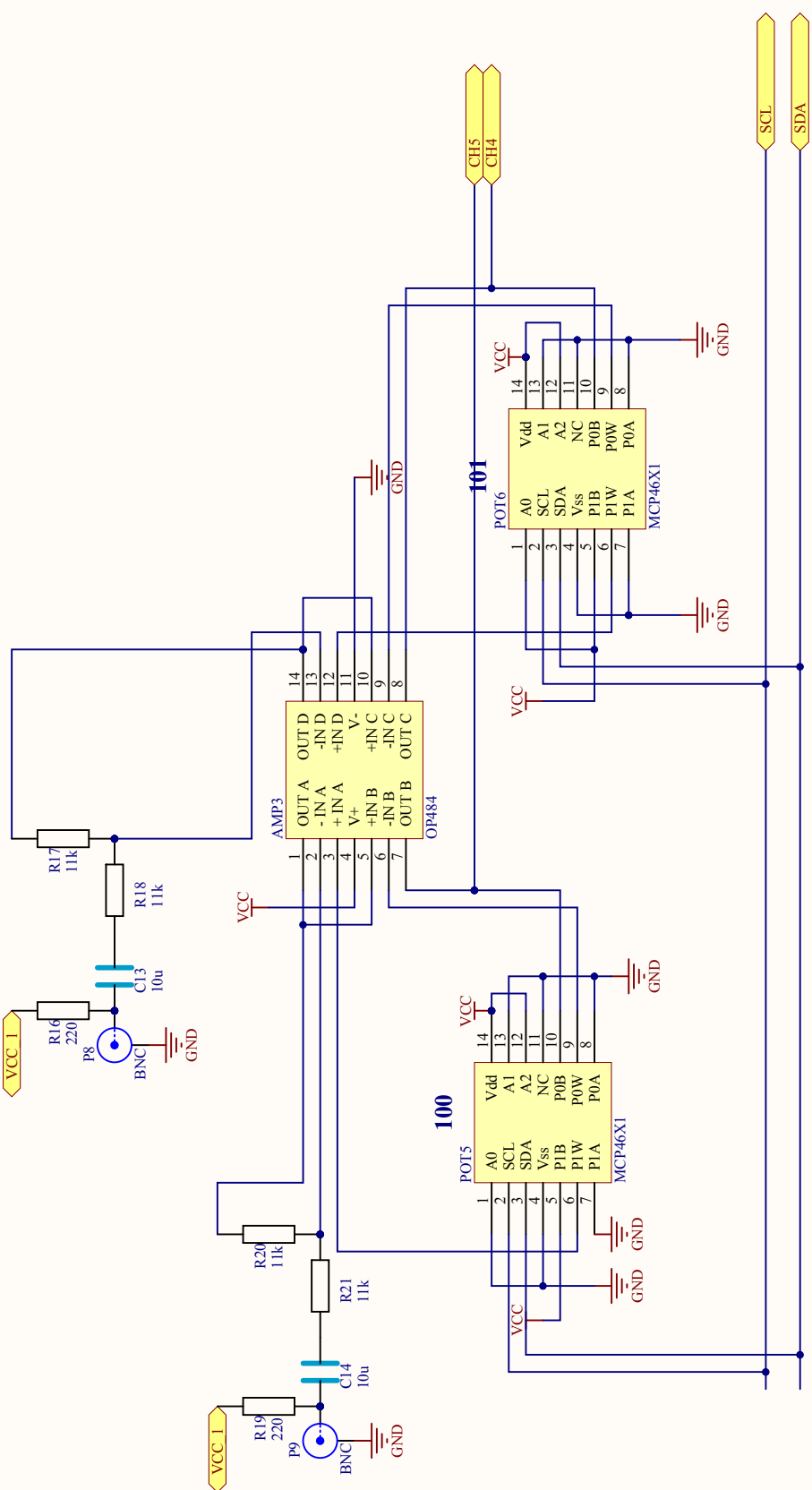

Title

Revision

Number

Size

A4

Date:

14.07.2014


File:

C:\Users\... \Sheet4_SchDoc

Sheet of

4

Drawn By:

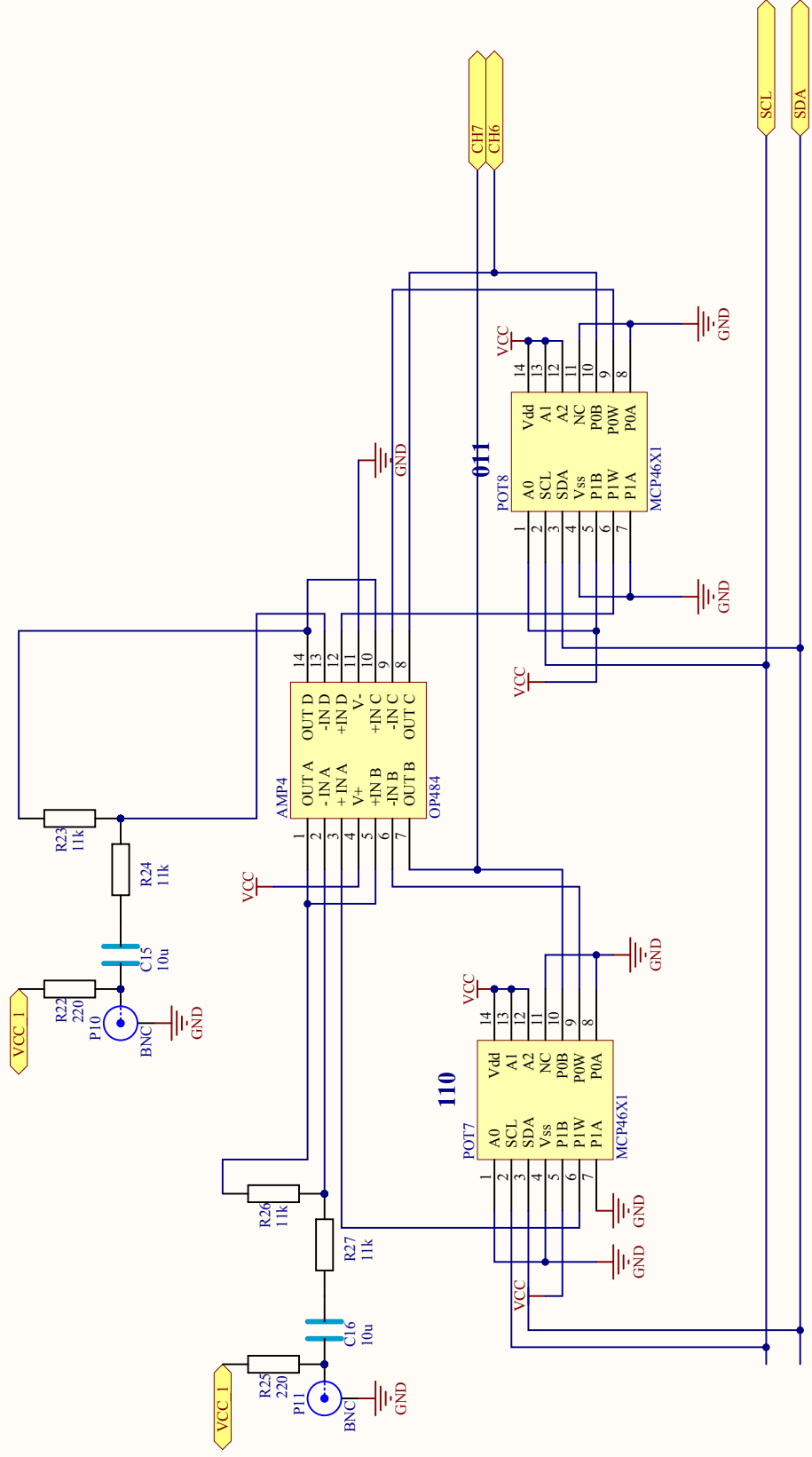

Title

Size

Number

Revision

A4

Date:

14.07.2014

Sheet of

4

File:

C:\Users\... \Sheet5_SchDoc


Drawn By:

A

B

C

D

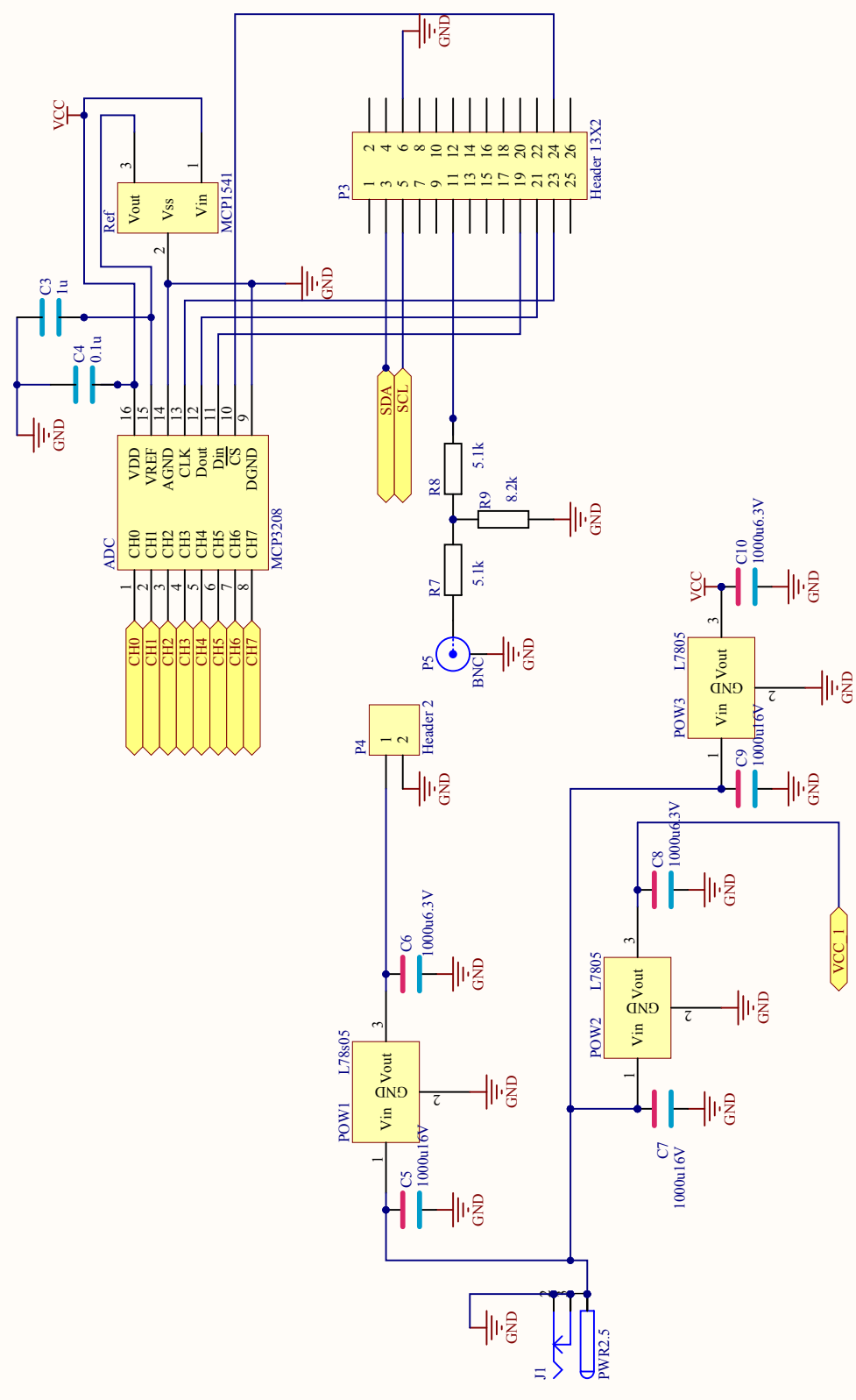

Title

Size	Number	Revision
A4		
Date:	14.07.2014	Sheet of
File:	C:\Users\... \Sheet2_SchDoc	Drawn By:

A

B

C

D

Comment	Description	Designator	Footprint	LibRef	Quantity
MCP3208	ADC, 12bit, 8ch, SPI	ADC	MCP3208	MCP3208	1
OP484	OP. AMP., quadrus	AMP1, AMP2, AMP3, AMP4	OP484	OP484	4
Capasitor	10u	C1, C2, C11, C12, C13, C14, C15, C16	RC	Capasitor	8
1u	1u	C3	RC	Capasitor	1
0.1u	0.1u	C4	RC	Capasitor	1
1000u16V	1000u 16V	C5, C9	C_b	C1000_16V	2
1000u6.3V	1000u 6.3V	C6, C8, C10	C_s	C1000_16V	3
	1000u 16V	C7	C_b	C1000_16V	1
PWR2.5	Low Voltage Power Supply Connector	J1	KLD-0202	PWR2.5	1
BNC	BNC Elbow Connector	P1, P2, P5, P6, P7, P8, P9, P10, P11	BNC_RA CON	BNC	9
Header 13X2	Header, 13-Pin, Dual row	P3	HDR2X13	Header 13X2	1
Header 2	Header, 2-Pin	P4	HDR1X2	Header 2	1
MCP46X1	Dig. Potentiometer, 256b, i2c	POT1, POT2, POT3, POT4, POT5, POT6, POT7, POT8	MCP46X1	MCP46X1	8
L78s05	Voltage Stab.	POW1	L78s05	L78s05	1
L7805	Voltage Stab.	POW2, POW3	L7805	L7805	2
Resistor	220, 11k, 11k, 220, 11k, 11k, 5.1k, 5.1k, 8.2k, 220, 11k, 11k, 220, 11k, 11k, 220, 11k, 11k, 220, 11k, 11k, 220, 11k, 11k, 220, 11k, 11k, 220, 11k, 11k	R1, R2, R3, R4, R5, R6, R7, R8, R9, R10, R11, R12, R13, R14, R15, R16, R17, R18, R19, R20, R21, R22, R23, R24, R25, R26, R27	RC	Resistor	27
MCP1541	Ref. Voltage Source	Ref	MCP1541	MCP1541	1